

AN11144

Universal Single LNB with TFF101x FIMOD IC

Rev 1.0 — 16 January 2012

Application note

Document information

Info	Content
Keywords	DNC, TFF101x, Ku Band, LNB
Abstract	The document provides circuit, layout, BOM and performance information for Ku Band Universal Single LNB equipped with NXP's TFF101x integrated DNC.



Revision history

Rev	Date	Description
1.0	20120116	First revision

Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction

TFF101x means a series of integrated Down-Converters (DNC) for Low Noise Block (LNB) at Ku band (10.7 GHz to 12.75 GHz) satellite receiver system. The family includes TFF1014, TFF1015, TFF1017 and TFF1018, in which the only difference is conversion gain.

TFF101x integrates most parts of Ku Band Universal Single (US) LNB, including pre-amplifier, mixer, buffer amplifier and PLL synthesizer, and the LO frequency (9.75GHz or 10.6GHz) can be easily switched by a logical level, so for a full US LNB, only an LNA, a 25MHz crystal and a biasing ICs are needed as the external circuits (As shown in Figure 1).

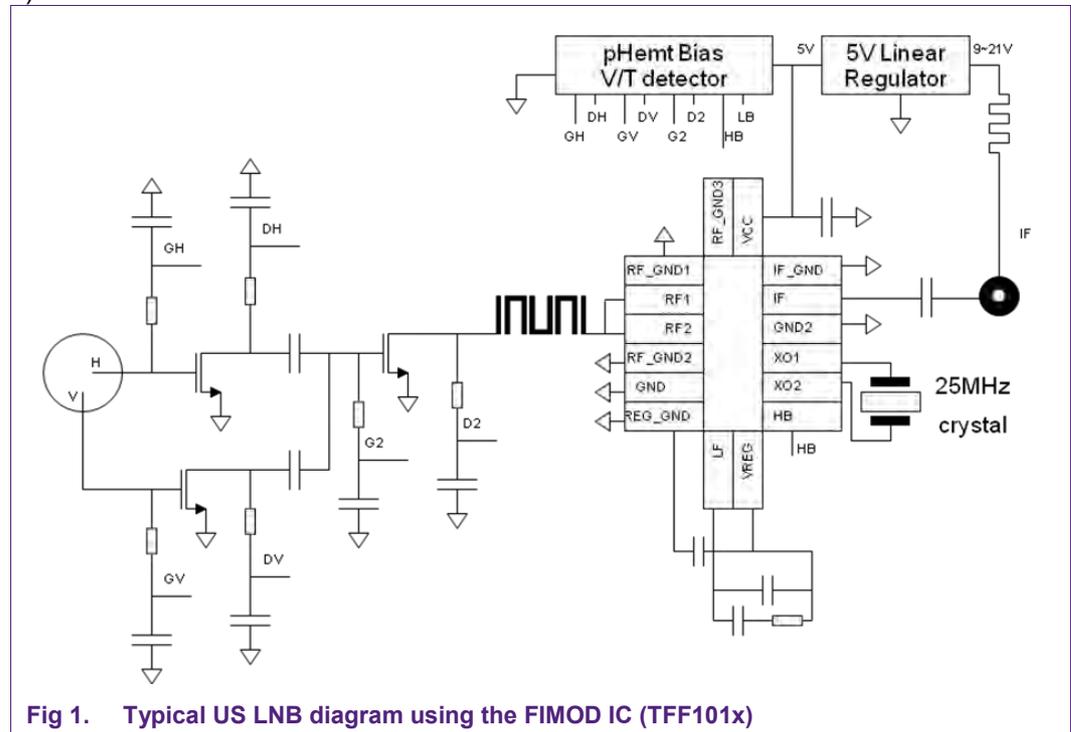


Fig 1. Typical US LNB diagram using the FIMOD IC (TFF101x)

TFF101x has excellent performance: Low noise figure (typ. 7dB), flat conversion gain (full band 1.4dB), low phase noise (1.5°RMS integrated from 10 kHz to 13 MHz), low power consumption (5V/52mA), good input (RF) and output (IF) return loss (>10dB). Since the DNC uses PLL synthesizer instead of DRO as the LO generator, the frequency accuracy utterly depends on the resonance frequency of crystal circuits, the LNB based on TFF101x is free of tuning, so both design and production become much easier.

This paper intends to describe a Ku band universal single LNB design which is used to evaluate the final performance when TFF101x is used in a real US LNB. It is well known that the LNA contributes the most NF (Noise Figure) of a total LNB, and the DNC contributes a smaller part of NF. To evaluate the final NF of a TFF101x LNB, a typical LNA with the popular transistor NE3503M04 is designed, and the relevant circuit parameters are given. The layout for TFF101x is discussed in detail, which is very important for NF, gain, phase noise and spurious suppression. The design files includes the schematic, layout, BOM, mechanical design are all presented then. To evaluate the reference design, both RF performance and signal quality are measured and compared with some discrete US LNBs in the market.

2. General Description

To evaluate the performance of TFF101x in a real US LNB, the design should be close to a real US LNB as much as possible. For convenience in RF measurement, the target prototype only differs from real US LNB in two points:

- The input interface is a circular waveguide (CWG) instead of a feed horn.
- The output interface is a 50Ω SMA connector instead of a 75Ω F type connector.

The LNA implemented in the LNB is a typical two-stage LNA based on NE3503M04, and in which, the power supply for the first stages are used for switching the polarization of vertical or horizontal.

Some performance like LO offset, phase noise and output power mainly depend on the performance of TFF101x, which has been well solved in single TFF101x EVB. The other performance like NF, gain flatness and image rejection mainly or partly depend on the external RF front-end. To make sure that the TFF101x LNB is satisfied with the current applications, the performance should be comparable with the available discrete LNBs in the market. The desired performance is shown in Table 1.

Table 1. Target Performance

Parameter		Value	Unit	Comments
Input Frequency	Low Band	10.70 to 11.70	GHz	
	High Band	11.70 to 12.75	GHz	
Output Frequency	Low Band	950 to 1950	MHz	
	High Band	1100 to 2150	MHz	
Local Oscillator Frequency	Low Band	9.75	GHz	
	High Band	10.6	GHz	
Phase Noise	At 10 kHz offset	-75	dBc/Hz	
Conversion Gain		55 to 70	dB	Depends on which TFF IC used
Gain Ripple		3	dB	
Noise Figure	Low Band	1.1	dB	Comparable with the discrete US LNB in the market
Image Rejection		40	dB	
1dB Compression Point		0	dBm	
3 rd Order Intermodulation		10	dBm	
Output Return Loss (50 Ω)		10	dB	
Cross Polar Rejection		20	dB	
Current Consumption		75	mA	

3. Design


The LNB consists of a base with CWG input, a cover for shielding, a PCBA with probes soldered. A fixture is made to assemble them precisely.

Since the Ku band LNB operates at very high frequency, the dimension of the base, cover, the probes and the assembly accuracy affect the NF and gain significantly. This information is given before the introduction of the circuits design.



The circuits design starts from the schematic design, after that, the simulation of the LNA and the Band Pass Filter (BPF) is presented. The layout for TFF101x is discussed in detail then, and in the end, the final PCB and the BOM are given.

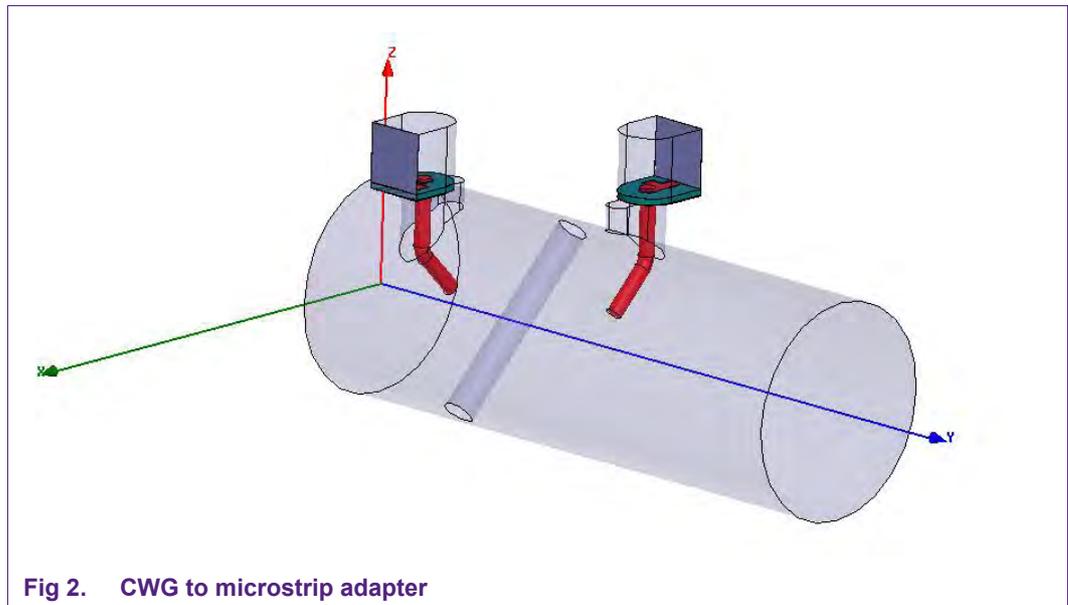3.1 Mechanical Design

The dimension of the CWG and the CWG to microstrip adapter (the probe) are very sensitive to the NF of the LNB. The impedance of the probes, including the input circuits of the LNA, are obtained by 3D EM simulation (the model is shown in Figure 2), and will be implemented in the simulation of LNA in [Section 3.3](#). The PCB material is Rogers 4003 with 20mil thickness, which has similar property with the special LNB laminates Rogers 4233, but more popular in PCB manufacturer.



The drawing of the base (including a short stick) and probes are shown in Figure 3 and Figure 4 respectively, and the dimensions of the CWG, probe and probe holes are based on the dimension in the model in Figure 2. It is also important to assemble the probe with right direction and position. To solder the probes precisely, a fixture is designed to position the probes during soldering, and the assembly process is shown in Figure 5.

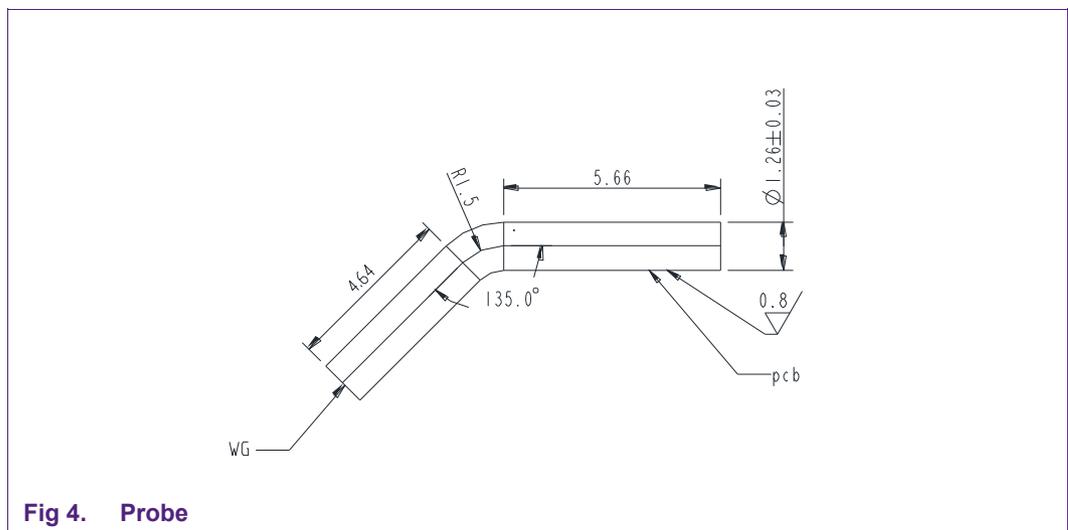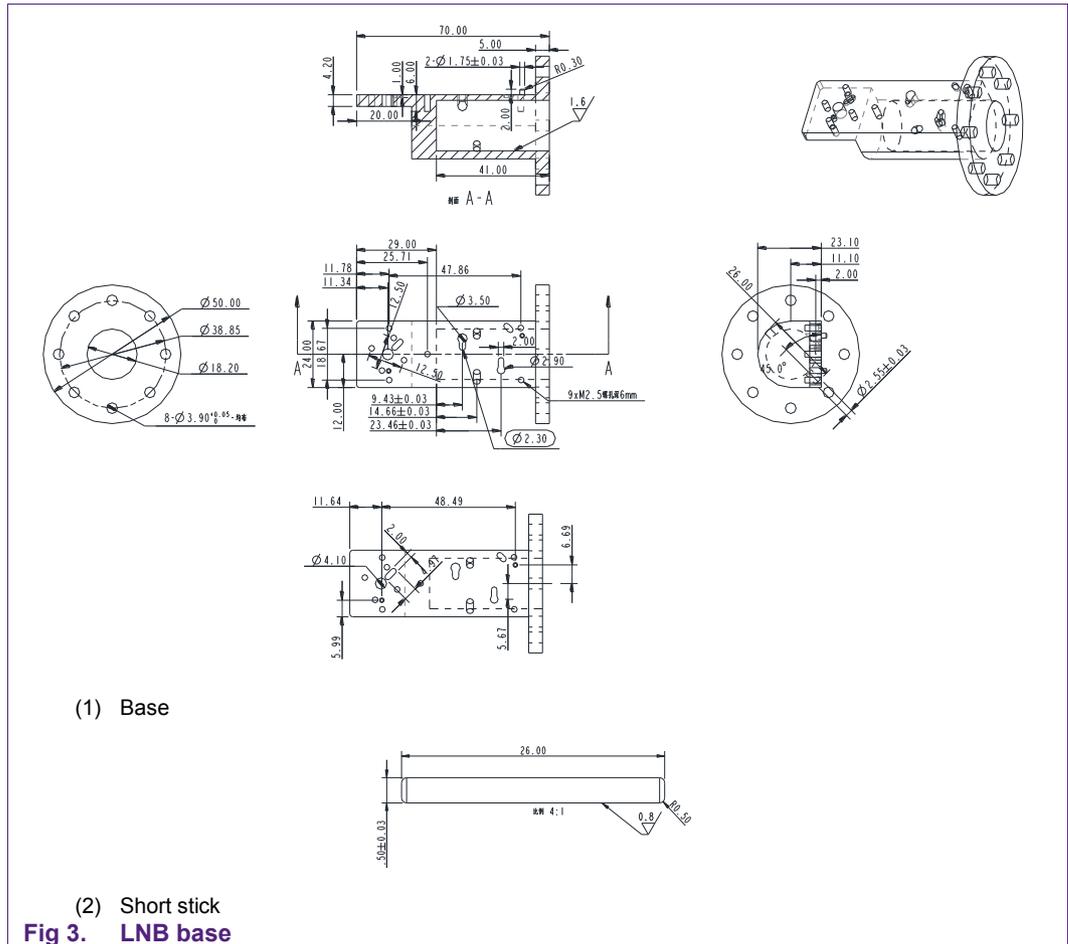

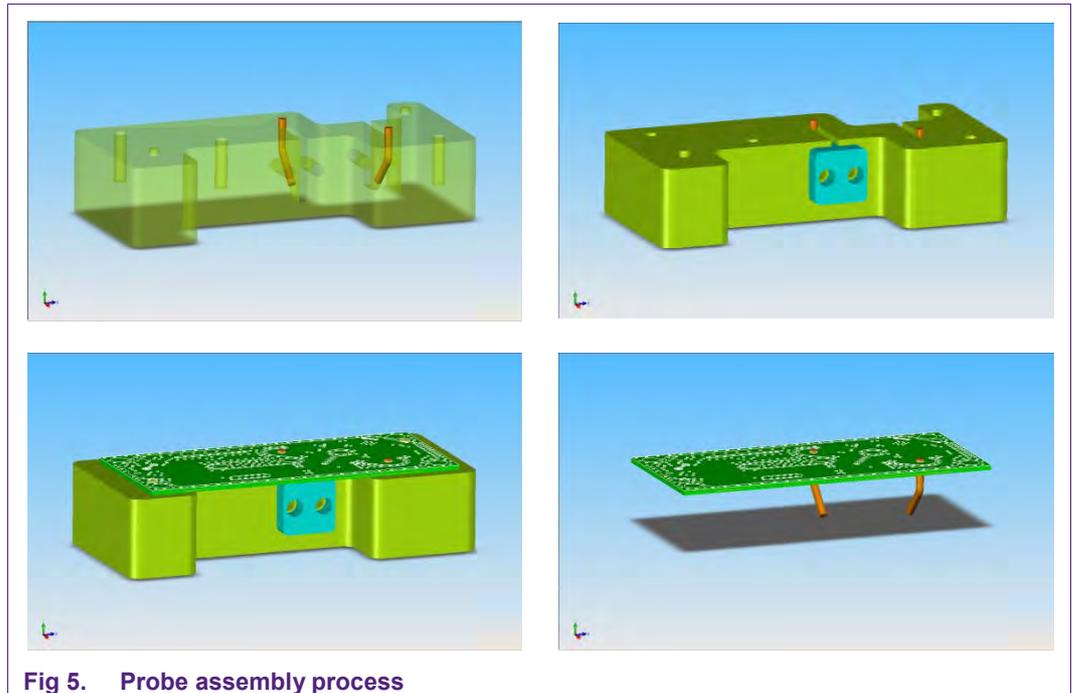


Fig 5. Probe assembly process

3.2 Schematic

The Schematic of the reference Ku band US LNB is shown in Figure 6.

Three pieces of NE3503M04 are used as the two-stage LNA for both vertical and horizontal polarization. ZXNB4202 is chosen as the voltage regulator and bias IC.

A JFVNY's 25MHz crystal is selected for the reference of the PLL. The overtone order is fundamental for stable temperature performance and the load capacitance is 8pF for accurate LO frequency.

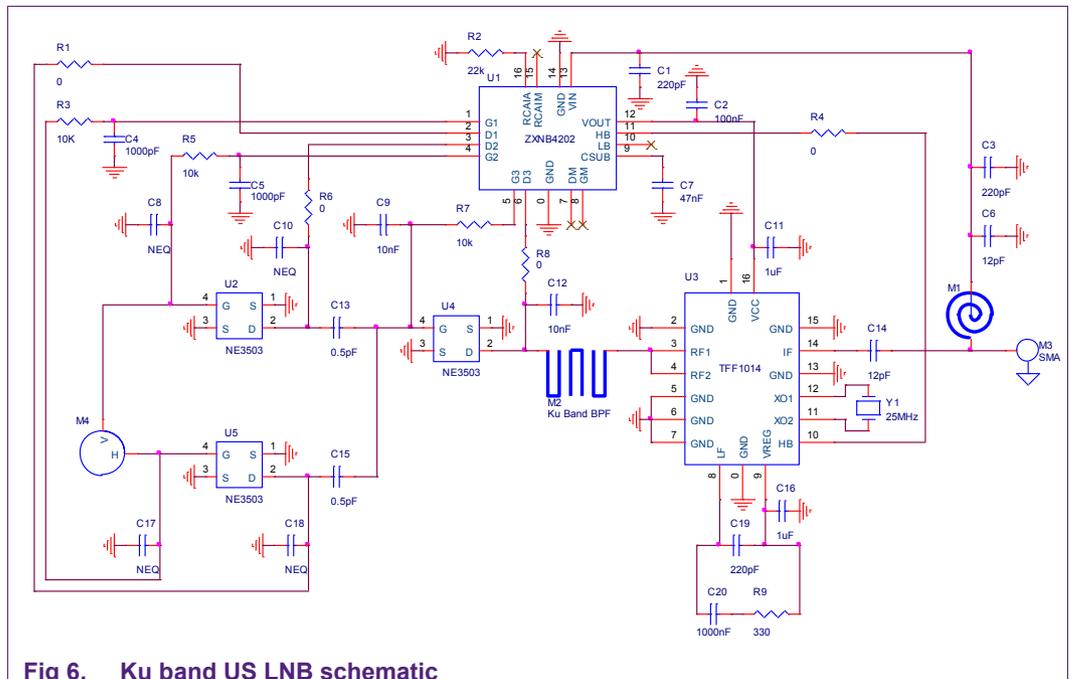


Fig 6. Ku band US LNB schematic

3.3 LNA and BPF Simulation

The LNA and BPF in Figure 6 is simulated and optimized for excellent NF, gain flatness and image rejection. The Simulation model is shown in Figure 7. SNP1 is the S parameters of the CWG to microstrip adapter, which is mentioned in Section 3.1. SNP2 and SNP3 is the de-embedding model to remove the effect of the overlapped parts in SNP1 and the NE3503 Model. The intermediate matching network, output matching network and the BPF are modeled by Momentum for better accuracy.

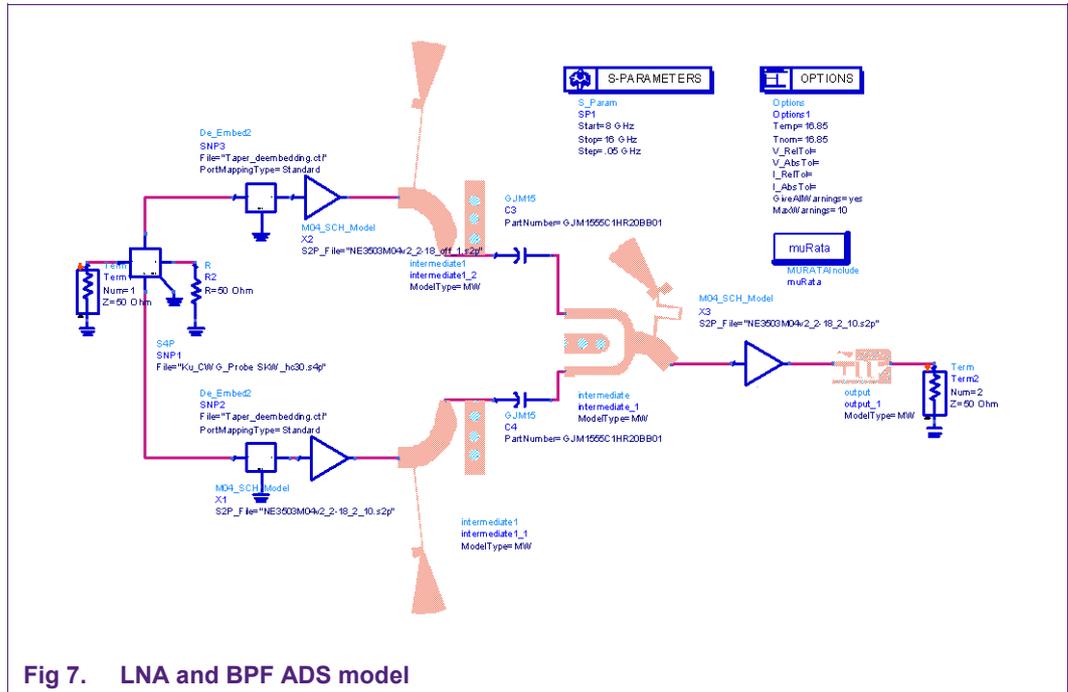


Fig 7. LNA and BPF ADS model

According to the simulation (the result is shown in Figure 8), the NF of both polarization paths, not taking account of the contribution of the DNC, is about 0.8dB. The total gain including the probe, the 2-stage-LNA and the image rejection BPF is about 20dB.

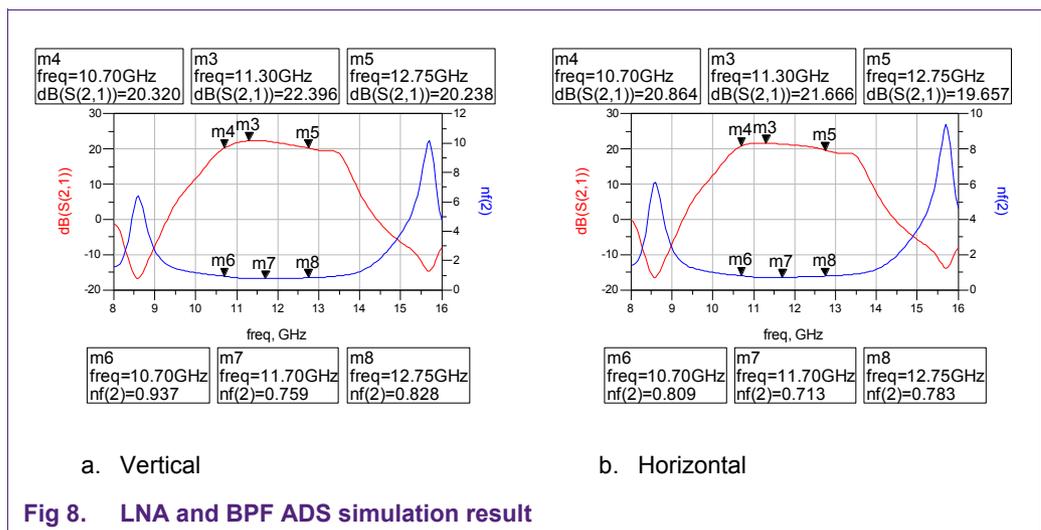


Fig 8. LNA and BPF ADS simulation result

3.4 Layout

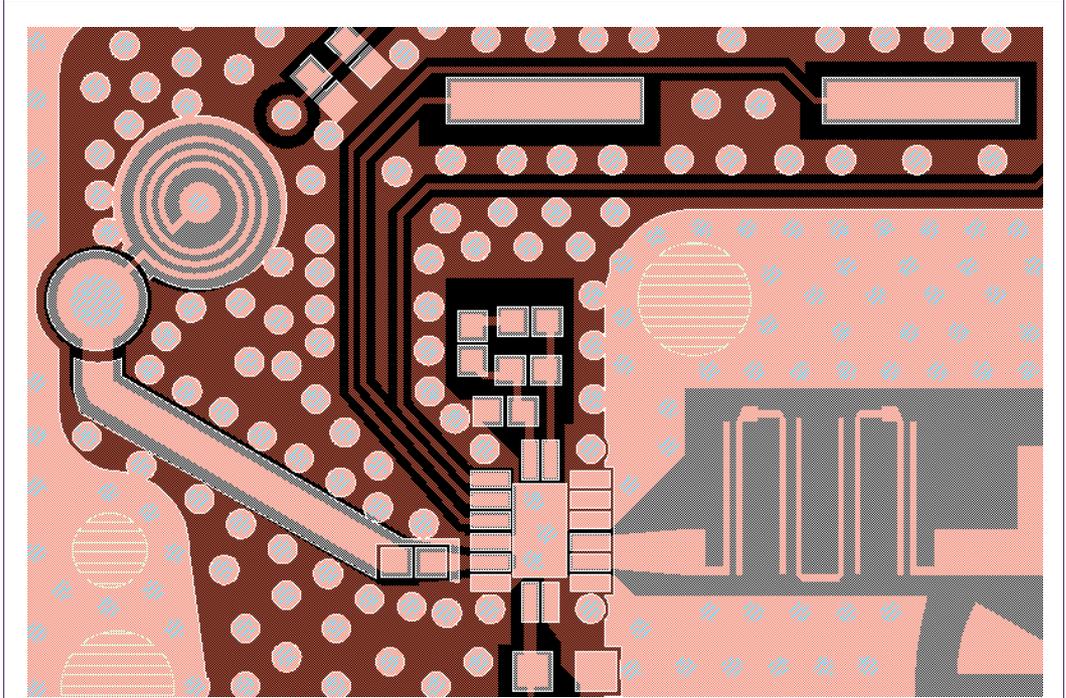


Fig 9. The footprint of TFF101x and surrounding circuits

The layout for TFF101x is zoomed and shown in Figure 9. There are some important points highlighted as follow.

- Grounds.
 - The die pad MUST be well grounded. There are three via, with 0.5 mm diameter, mapped directly on the die pad.
 - GND via should be put as close as possible to the other GND pins.
 - It is strongly recommended to copy all the GND via in and surrounding TFF101x to any practical design.
- Footprint.
 - Die pad size: 2x1 mm. And soldering mask is 0.1mm larger for each side.
 - Other pads 0.85x0.3mm, slightly bigger than the pins for easier soldering. And the soldering mask is 0.05mm larger for each side.
 - It is strongly recommended to copy the footprint of TFF101x to any practical design.
- RF input.
 - 50 Ω transmission line which has been used in TFF101x EVB before is used here again.
- IF line.
 - 50 Ω Coplanar Waveguide with Ground (CPWG) line for good matching and anti-interference. The width of the CPWG line is 20mil, which is identical with the width of a 0402 capacitor.

- Decoupling capacitors.
 - There two decoupling capacitors for TFF101x: one is for VCC and the other is for VREG. Both should be placed as close as possible to the power pins.
- Loop filter.
 - The area of the loop filter (LF) should be as small as possible.
 - There is a GND ring surrounding the LF, for shielding the interference.
- 25MHz crystal.
 - The pair of 25MHz lines goes parallel like differential lines for better anti-interference.
 - The gap between the 25MHz lines, as well as their width, should be as thin as possible (both are 0.15mm actually).
 - As much as GND on both side of the 25MHz lines

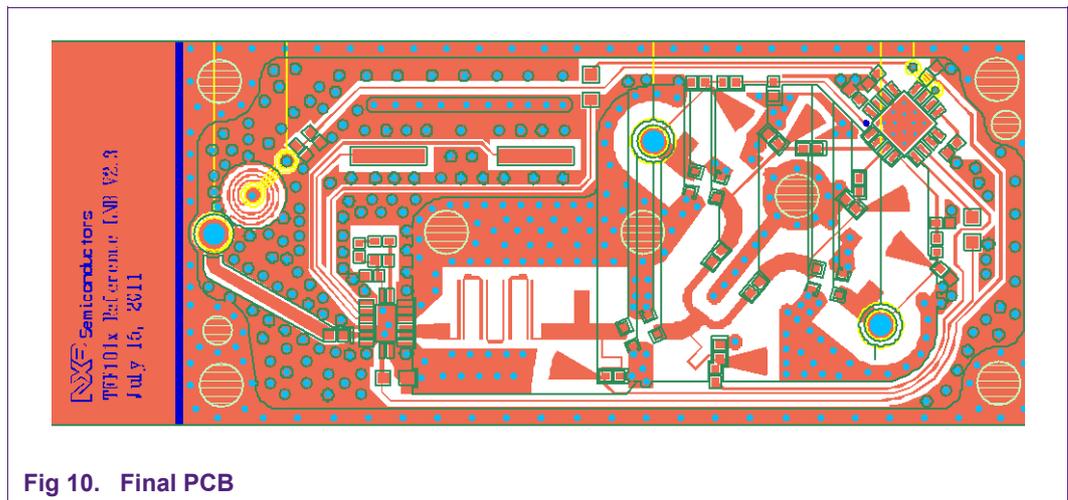


Fig 10. Final PCB

The final PCB layout is shown in Figure 10. The maroon filled patterns are the top layer, the golden outlines are the bottom layout, the light blue filled circles are plated via, the white shadowed circles are non-plated holes for mounting, and the white outline is the soldering mask layer.

3.5 Bill of Materials

Table 2. Bill of materials

Designator	Description	Footprint	Qty	Value	Supplier Name/type
U1	Bias IC	QFN1644	1		ZETEX -ZXNB4202JB16TC
U2,U4,U5	HJFET	SOT343	3		Renesas-NE3503M04
U3	FIMOD	DHVQFN16	1		NXP -TFF1014N1
C1,C3,C19	Capacitor	0402	3	220pF	Murata-GRM1555C1H221J

Designator	Description	Footprint	Qty	Value	Supplier Name/type
C2,C20	Capacitor	0402	2	0.1uF	Murata-GRM155R71C104K
C4,C5	Capacitor	0402	2	1000pF	Murata-GRM155R71H102K
C6,C14	Capacitor	0402	2	12pF	Murata-GRM1555C1H120J
C7	Capacitor	0402	1	47nF	Murata-GRM155R71E473K
C9,C12	Capacitor	0402	2	10nF	Murata-GRM155R71H103K
C11	Capacitor	0603	1	1uF	Murata-GRM188R61A105K
C13,C15	Capacitor	0402	2	0.5pF	Murata-GJM1555C1HR50B
C16	Capacitor	0402	1	1uF	Murata-GRM155R61A105K
R1,R6	Resistor	0402	2	0	Ralec-RTT02000J
R2	Resistor	0402	1	22k	Ralec-RTT022202F
R3,R5,R7	Resistor	0402	3	10k	Ralec-RTT021002F
R4,R8	Resistor	0603	2	0	Ralec-RTT03000J
R9	Resistor	0402	1	330	Ralec-RTT023300F
Y1	Crystal	HC-49XA	1	25MHz	JFVNY-HC-49XA-C08TTA-25.000MHz

3.6 LNB View



Fig 11. LNB view

4. Measured Results

The items in Table 1 are measured and given in [Section 4.1](#), while the live signal test has also been implemented and results is shown in [Section 4.2](#).

4.1 General Performance

Five US LNBs have been made. LNB #1 and #2 are based on TFF1015, #3 is based on TFF1017, #4 is based on TFF1014, and #5 is based on TFF1018. The conversion gain of different type of DNC is compared in [Section 4.1.1](#). And in [Section 4.1.2](#), The NF curves of all the LNBs, as well as that of two discrete LNBs from W Company and S Company as the benchmark, are given. The plots of the phase noise and output return loss are shown in [Section 4.1.3](#) and [Section 4.1.4](#) respectively. All the measured specifications are summarized in [Section 4.1.5](#).

4.1.1 Conversion Gain

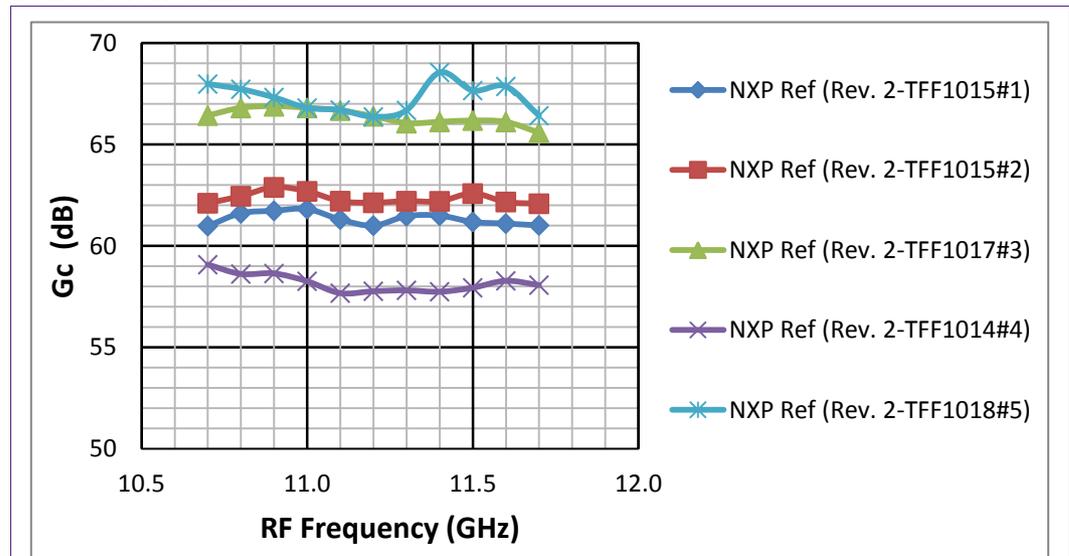


Fig 12. Conversion gain measurement results (Low band/Vertical)

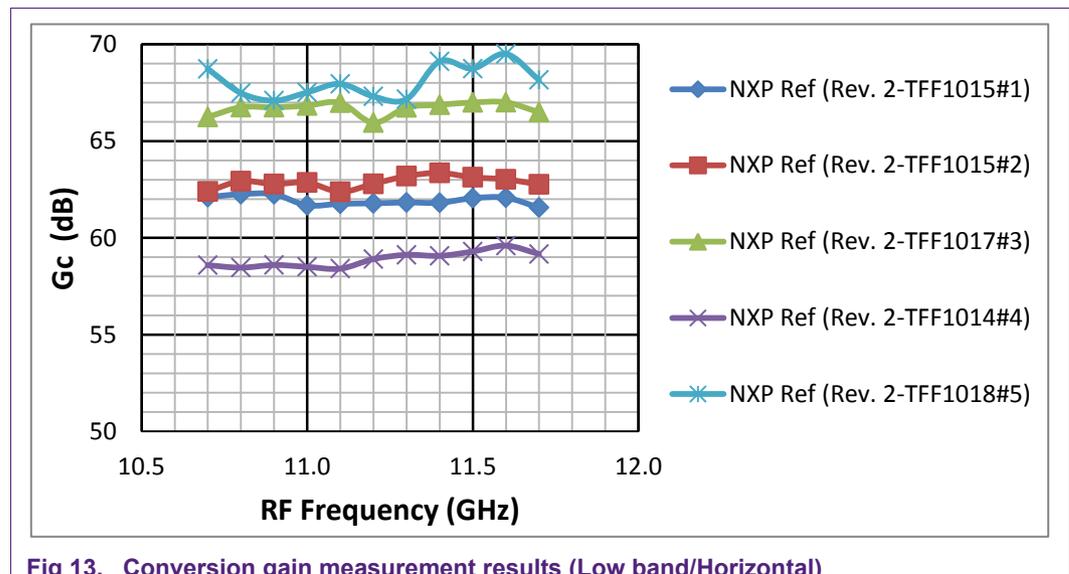


Fig 13. Conversion gain measurement results (Low band/Horizontal)

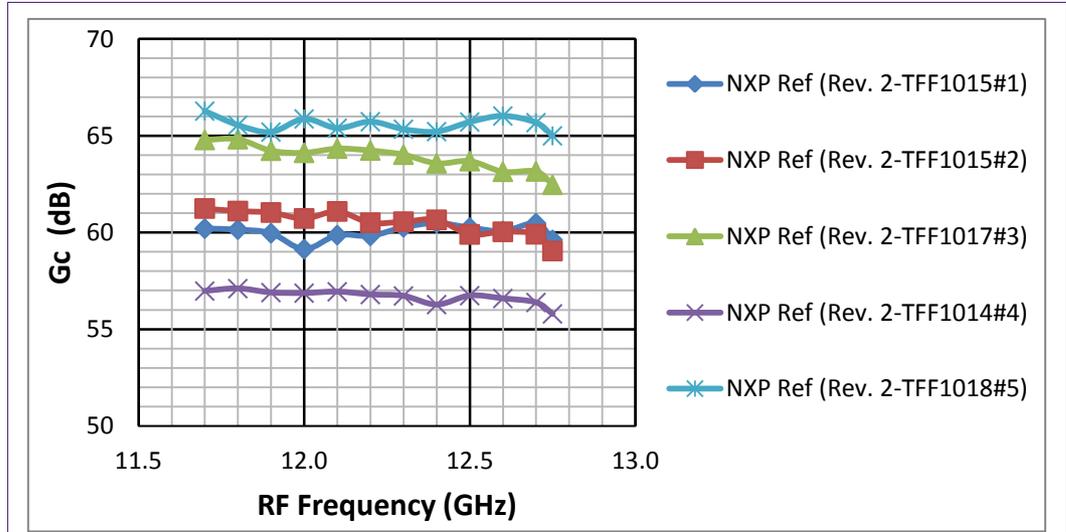


Fig 14. Conversion gain measurement results (High band/Vertical)

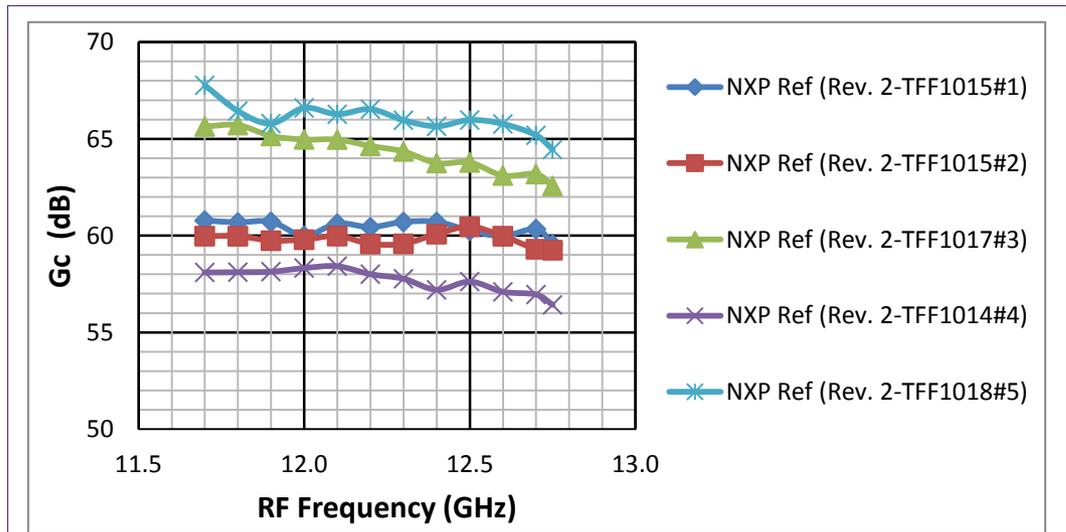


Fig 15. Conversion gain measurement results (High band/Horizontal)

As shown in Figure 12 to Figure 15, the conversion gain of LNB with TFF1014 is 58dB and 57dB at low band and high band respectively; for TFF1015 LNB, these values are 62dB and 60dB respectively; for TFF1017 LNB, they are 66db and 64dB; and for TFF1018 LNB, they are 68dB and 66dB.

4.1.2 Noise Figure

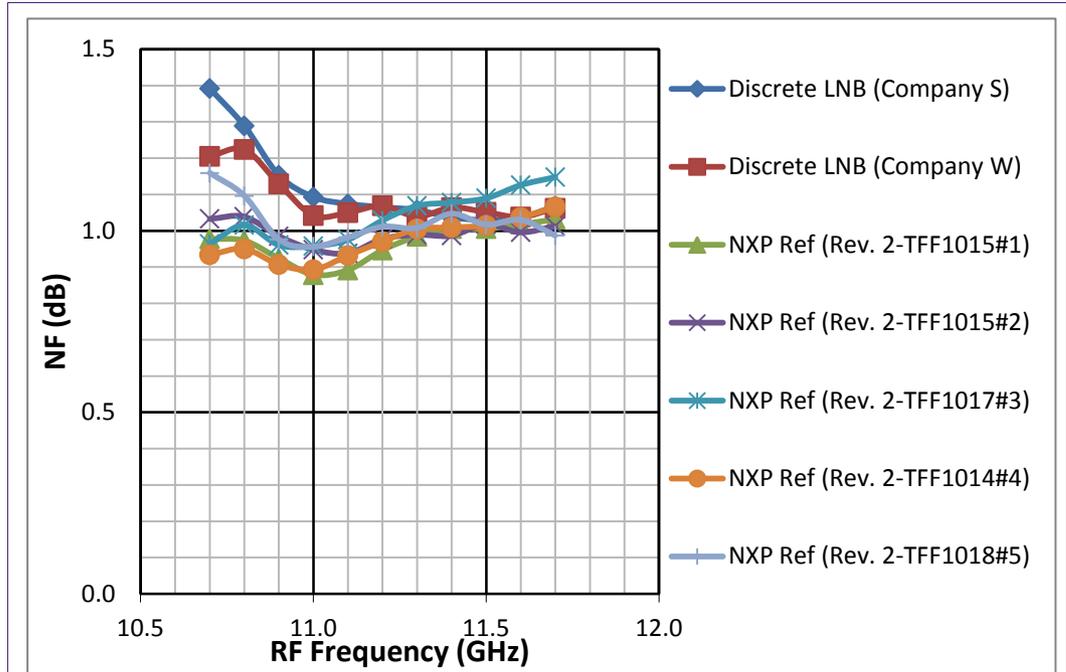


Fig 16. Noise figure measurement results (Low band/Vertical)

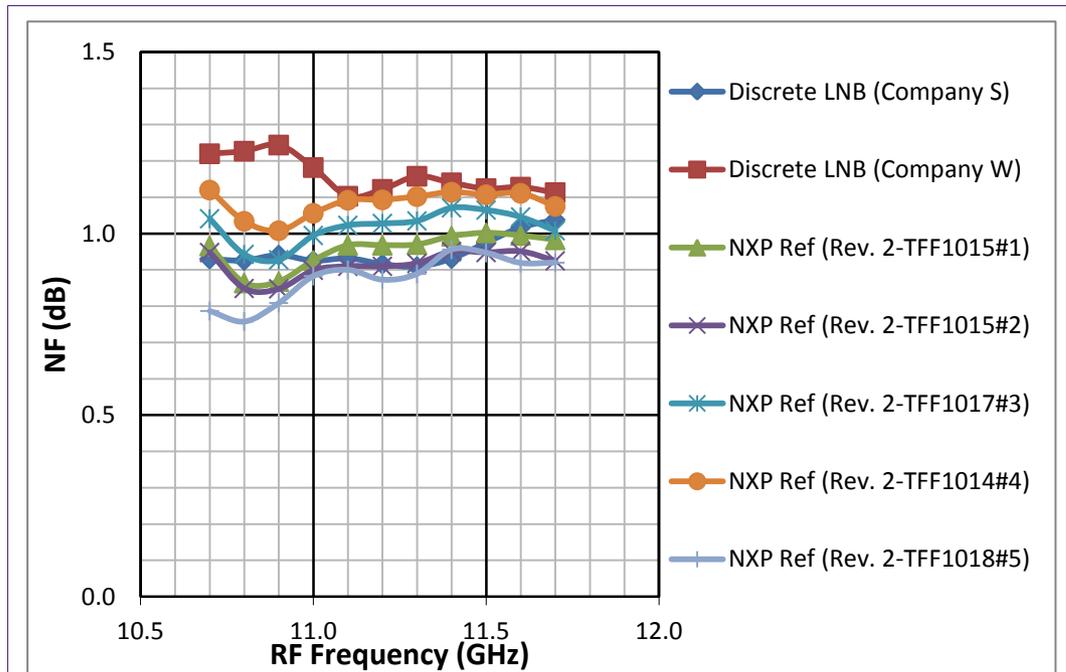


Fig 17. Noise figure measurement results (Low band/Horizontal)

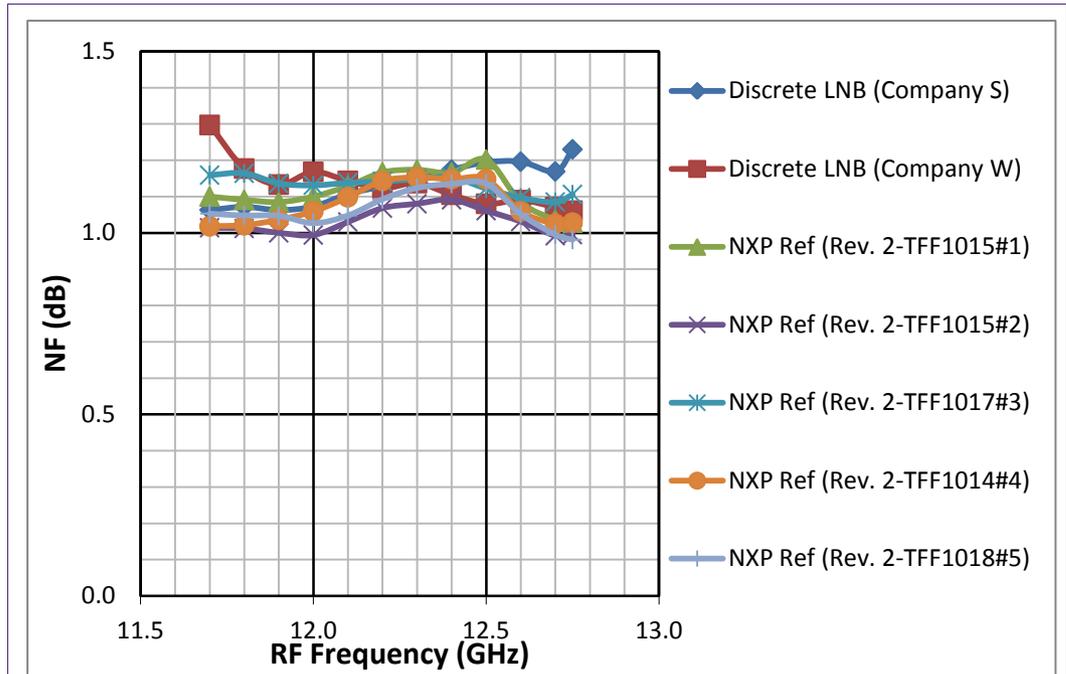


Fig 18. Noise figure measurement results (High band/Vertical)

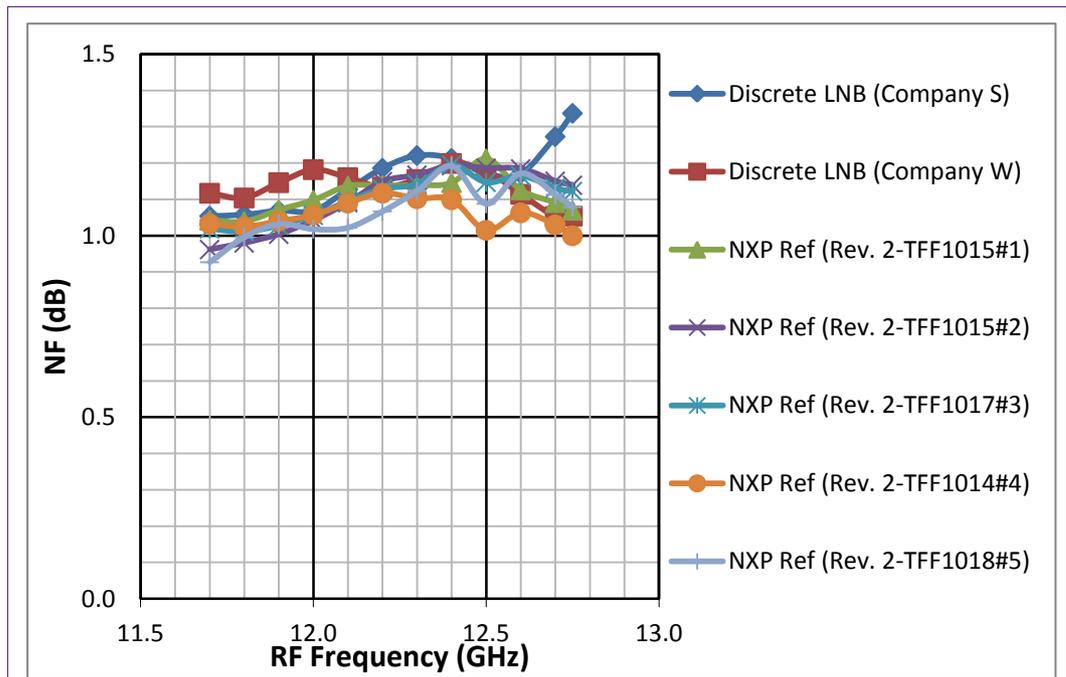


Fig 19. Noise figure measurement results (High band/Horizontal)

The NF of all the NXP US LNBs are plotted in Figure 16 to Figure 19 for low band and high band respectively, and as a reference, the NF of discrete LNBs of S Company and W Company, measured in the same system, is also given for comparison.

The NF of all the LNB based on TFF101x is comparable with that of discrete LNB. The NF is about 1.0dB at low band and 1.1dB at high band. The worst NF in the full band is no worse than 1.2dB.

4.1.3 Phase Noise

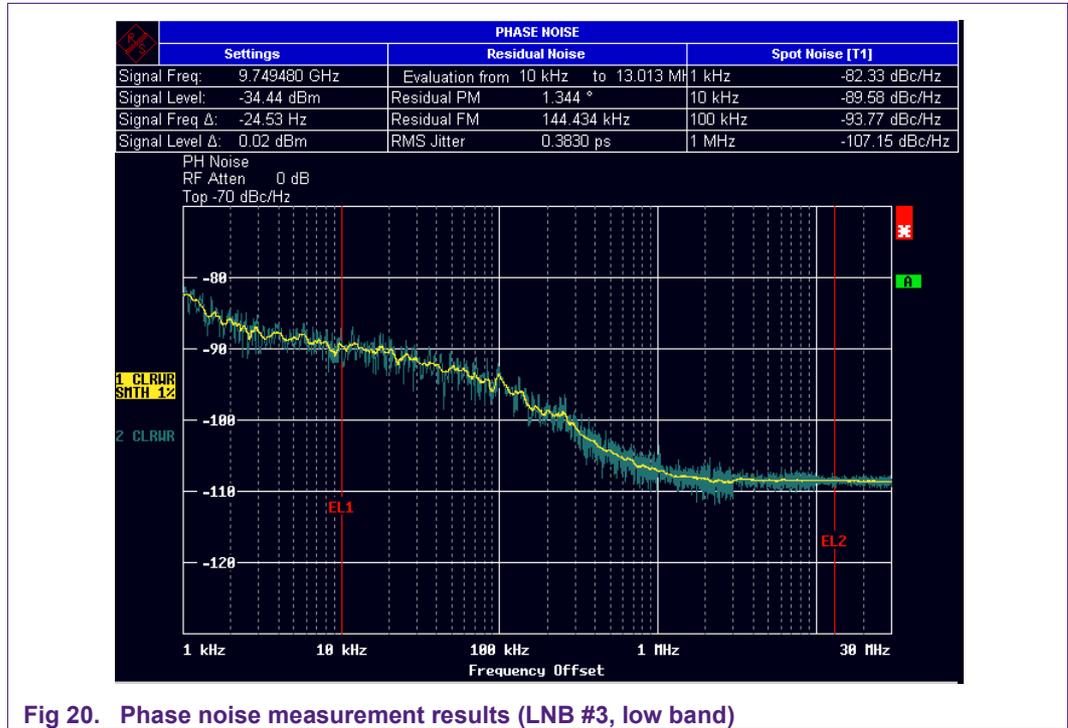


Fig 20. Phase noise measurement results (LNB #3, low band)

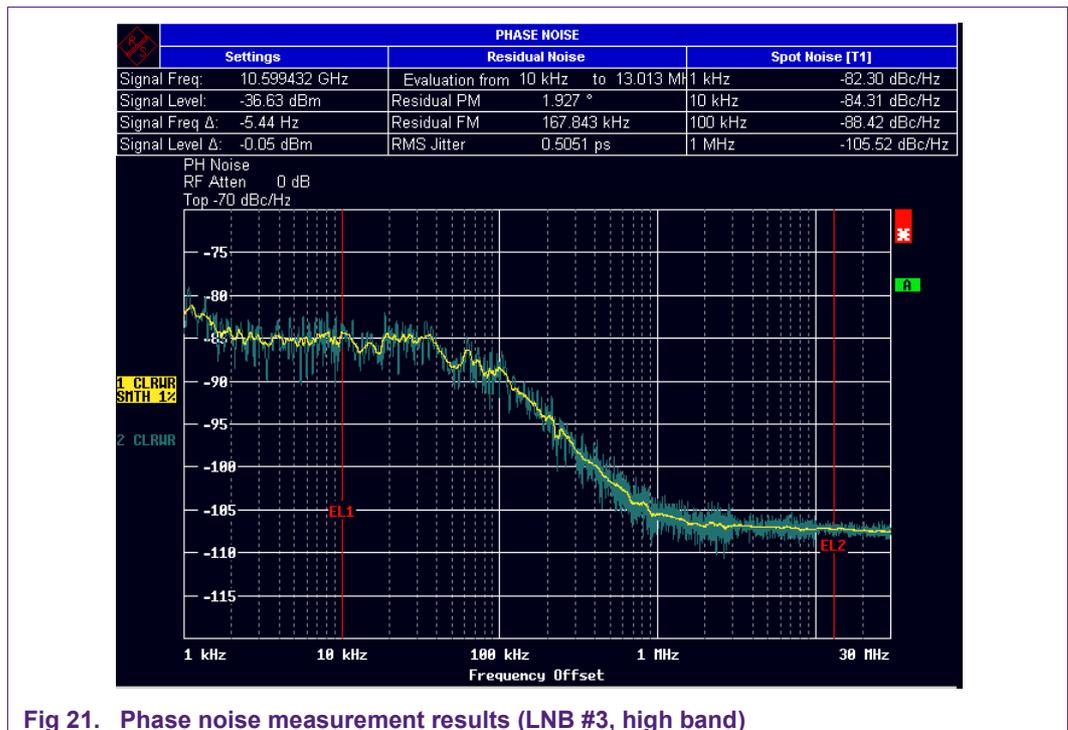


Fig 21. Phase noise measurement results (LNB #3, high band)

The #3 LNB based on TFF1017 is selected for the phase noise test, because the LO (Local Oscillator) magnitude leakage to IF port of the other LNBS is too small to measure the far end phase noise accurately. The phase noise (Figure 20) of 9.75GHz LO is -82, -90, -94, and -107dBc/Hz at 1k, 10k, 100k, 1MHz respectively, and those for 10.6GHz LO (Figure 21) is -81, -84, -88, -106dBc/Hz. The LO offset is about -500kHz.

4.1.4 Output Return Loss

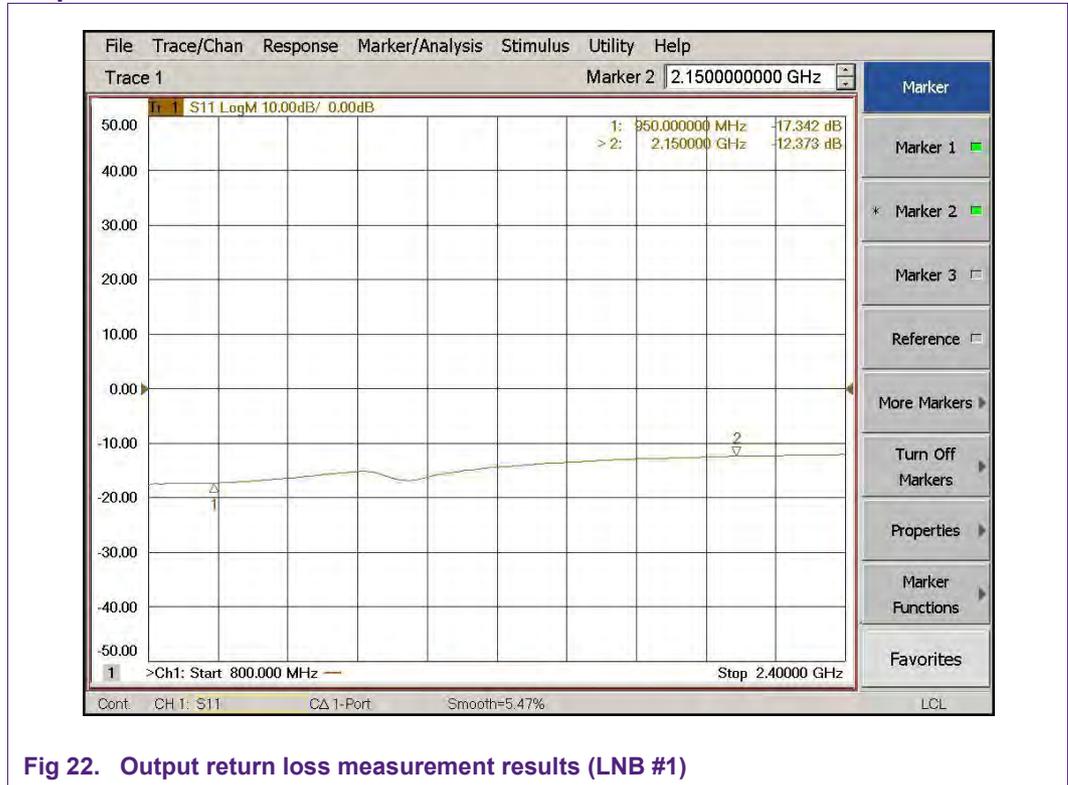


Fig 22. Output return loss measurement results (LNB #1)

As shown in Figure 22, the worst output return loss (for 50 Ω, only for reference) is -12dB.

4.1.5 Summary

Corresponding to the specification in Table 1, the items are measured and filled into Table 3. All the specifications reach the targets, or even better.

Table 3. Expected and Measured Results

Parameter		Expected	Measured	Unit	Comments
Local Oscillator Frequency	Low Band	9.750000	9.749499	GHz	500kHz offset
	Low Band	9.750000	9.749499	GHz	
Phase Noise	At 10 kHz offset	-75	-90 to -85	dBc/Hz	
Conversion Gain	TFF1014	LB	58		55 to 70 dB
		HB	57		
	TFF1015	LB	62		
		HB	60		
	TFF1017	LB	66		
		HB	64		
TFF1018	LB	68			
	HB	66			
Gain Ripple		3	3 (Max.)	dB	
Noise Figure	Low Band	1.1	1.0	dB	Comparable with the discrete US LNB in the market
	High Band	1.3	1.1	dB	

Parameter	Expected	Measured	Unit	Comments
Image Rejection	40	~56	dB	tested at 9.5GHz (image of 11.7GHz for HB)
1dB Compression Point	0	4.1	dBm	IF=2150 MHz
3 rd Order Intermodulation	10	18 (Min.)	dBm	IF=2000 MHz
Output Return Loss	10	12	dB	For 50 Ω
Cross Polar Rejection	20	20	dB	at 12.75GHz
Current Consumption	75	75 (Typ.)	mA	

4.2 Signal Quality

The #2 NXP reference LNB is mounted on a Rover (approx 2 meters) 60cm triax parabolic antenna to receive the signal from satellite of Astra 19.2^E, and the Modulation Error Ratio (MER) is measured (the weather condition of almost blue sky, temperature approximately 5°C) and shown in Figure 23. The MER of 8PSK and QPSK are both around 14dB, which meets Astra’s requirement.

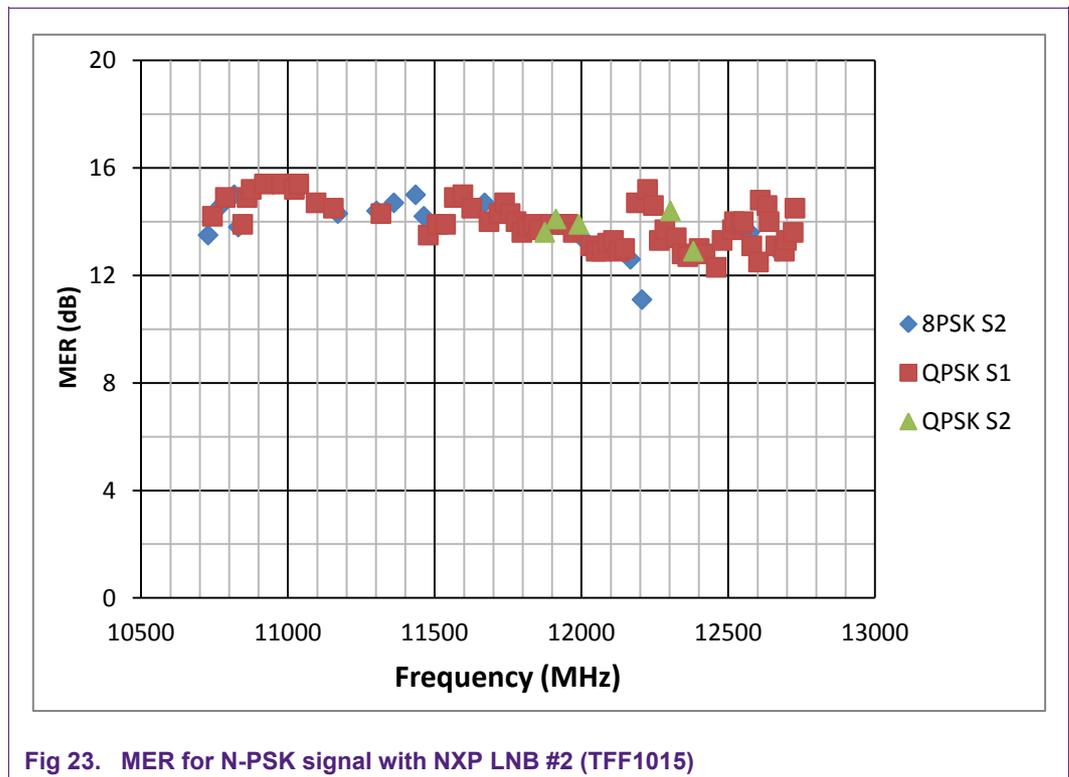


Fig 23. MER for N-PSK signal with NXP LNB #2 (TFF1015)

5. Conclusions

A design of Ku band universal single LNB based on TFF101x has been made, and all specification match the requirement for DVB-S application.

6. Legal information

6.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

6.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine

whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

6.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are property of their respective owners.

<Name> — is a trademark of NXP B.V.

7. List of figures

Fig 1.	Typical US LNB diagram using the FIMOD IC (TFF101x)	3
Fig 2.	CWG to microstrip adapter.....	5
Fig 3.	LNB base	6
Fig 4.	Probe	6
Fig 5.	Probe assembly process.....	7
Fig 6.	Ku band US LNB schematic.....	7
Fig 7.	LNA and BPF ADS model	8
Fig 8.	LNA and BPF ADS simulation result	8
Fig 9.	The footprint of TFF101x and surrounding circuits.....	9
Fig 10.	Final PCB.....	10
Fig 11.	LNB view.....	11
Fig 12.	Conversion gain measurement results (Low band/Vertical).....	12
Fig 13.	Conversion gain measurement results (Low band/Horizontal).....	12
Fig 14.	Conversion gain measurement results (High band/Vertical).....	13
Fig 15.	Conversion gain measurement results (High band/Horizontal).....	13
Fig 16.	Noise figure measurement results (Low band/Vertical).....	14
Fig 17.	Noise figure measurement results (Low band/Horizontal).....	14
Fig 18.	Noise figure measurement results (High band/Vertical).....	15
Fig 19.	Noise figure measurement results (High band/Horizontal).....	15
Fig 20.	Phase noise measurement results (LNB #3, low band).....	16
Fig 21.	Phase noise measurement results (LNB #3, high band).....	16
Fig 22.	Output return loss measurement results (LNB #1).....	17
Fig 23.	MER for N-PSK signal with NXP LNB #2 (TFF1015).....	18

8. List of tables

Table 1. Target Performance4
Table 2. Bill of materials..... 10
Table 3. Expected and Measured Results 17

9. Contents

1.	Introduction	3
2.	General Description	4
3.	Design	5
3.1	Mechanical Design	5
3.2	Schematic	7
3.3	LNA and BFP Simulation	8
3.4	Layout	9
3.5	Bill of Materials	10
3.6	LNB View	11
4.	Measured Results.....	12
4.1	General Performance	12
4.1.1	Conversion Gain	12
4.1.2	Noise Figure.....	14
4.1.3	Phase Noise.....	16
4.1.4	Output Return Loss	17
4.1.5	Summary.....	17
4.2	Signal Quality	18
5.	Conclusions	18
6.	Legal information	19
6.1	Definitions	19
6.2	Disclaimers.....	19
6.3	Trademarks.....	19
7.	List of figures.....	20
8.	List of tables	21
9.	Contents.....	22

Please be aware that important notices concerning this document and the product(s) described herein, have been included in the section 'Legal information'.

© NXP B.V. 2011.

All rights reserved.

For more information, visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 16 January 2012

Document identifier: AN11144